

# Counters

CS207 Chapter A

James YU

yujq3@sustech.edu.cn

Department of Computer Science and Engineering  
Southern University of Science and Technology

Dec. 7, 2022



南方科技大学  
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY




# Counters

- Counters are one of the simplest types of sequential networks.
- A counter is usually constructed from one or more flip-flops that change state in a prescribed sequence when input pulses are received.
- Since the clock pulses occur at known intervals, the counter can be used as **an instrument for measuring time** and therefore period of frequency.
  - Asynchronous and synchronous counters.
  - Single and multimode counters.
  - Modulus counters.
 
# Aynchronous counters



- A.k.a. *Serial* or *ripple counters*.
- The simplest counter circuit can be built using T flip-flops because the toggle feature is naturally suited for the implementation of the counting operation.
- All the flip-flops are not driven by the same clock pulse.
  - The successive flip-flop is triggered by the output of the previous flip-flop.
  - Hence the counter has cumulative settling time, which limits its speed of operation.



 
# Aynchronous counters



A **cascade** is a waterfall.

- The clock inputs of the three flip-flops are connected **in cascade**.
- The T input of each flip-flop is **connected to a constant 1**, which means that the state of the flip-flop will toggle (reverse) at each **negative edge** of its clock.
- We are assuming that the purpose of this circuit is to count the number of pulses that **occur on the primary input CLK (Clock)**.
- Thus the clock input of the first flip-flop is connected to the CLK line.





# Asynchronous counters

- The counter has 8 different states.
  - It is a MOD-8 asynchronous counter.
- The Modulus (or MOD-number) of a counter is the total number of unique states it passes through in each of the complete cycles.
- The maximum binary number that can be counted by the counter is  $2^n - 1$ .

represented by N

state

State	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

# Asynchronous counters



- The input consists of a sequence of pulses of frequency  $f$ .
- $Q_0$  changes only when the clock makes a transition from 1 to 0.
  - Two input pulses will result in a single pulse in  $Q_0$ .
  - The frequency of  $Q_0$  is  $f/2$ .
- Similarly, the frequency of  $Q_1$  signal will be half that of  $Q_0$  signal, i.e.,  $f/4$ .
- The frequency of  $Q_2$  signal will be half that of  $Q_1$  signal, i.e.,  $f/8$ .
- **Frequency divider.**
  - If there are  $n$  flip-flops used in the circuit then the frequency will be divided by  $2^n$ .

State	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

The frequency of  $Q_0$  is already different from the original clk, as  $Q_0$  is activated at the POSEDGE of the clk


# Asynchronous counter with modulus $< 2^n$



- In practice, it is often required to have a counter which has a MOD-number less than  $2^n$ .
- In such cases, it is required that the counter will skip states that are normally a part of the counting sequences.

the number of unique state

way to achieve this purpose

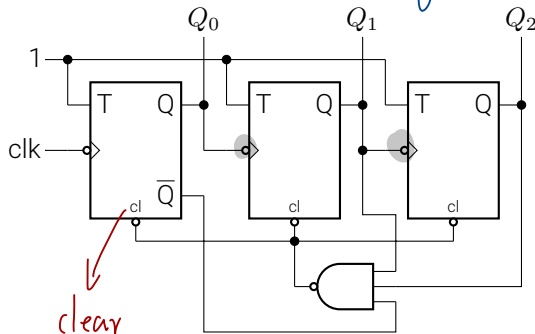



 
# Asynchronous counter with modulus $< 2^n$



- Although the counter goes to the 110 state, it remains there only for a few nanoseconds before it recycles to the 000 state.
- Hence we may say that the counter counts from 000 to 101, it skips the states 110 and 111.
- Works as a MOD-6 counter.




# Asynchronous counter with modulus $< 2^n$



- To construct any MOD- $N$  counter, the following general steps are to be followed.
  - Find the number of flip-flops  $n$  required for the desired MOD-number using the equation  $2^{n-1} < N < 2^n$ .
  - Then connect all the  $n$  flip-flops as a ripple counter.
  - Find the binary number for  $N$ .
  - Connect all the flip-flop outputs, for which  $Q = 1$ , as well as  $Q' = 1$ , when the count is  $N$ , as inputs to the NAND gate.
  - Connect the NAND gate output to the clear input of each flip-flop.
- When the counter reaches the  $N$ -th state, the output of the NAND gate goes low, resetting all flip-flops to 0.  
*as there has a bubble before cl.*

 
# Asynchronous down-counter

- A *down-counter* using  $n$  flip-flops counts downward starting from a maximum count of  $2^n - 1$  to zero.
- Such a down-counter may be designed in three different ways as follows.


 
# Asynchronous down-counter

- A *down-counter* using  $n$  flip-flops counts downward starting from a maximum count of  $2^n - 1$  to zero.
- Such a down-counter may be designed in three different ways as follows.




# Asynchronous down-counter

- A *down-counter* using  $n$  flip-flops counts downward starting from a maximum count of  $2^n - 1$  to zero.
- Such a down-counter may be designed in three different ways as follows.

this design way is easier to understand.

 for a down counter, only when the LSB change from 0 to 1, the MSB is needed to change. So the clk of the MSB change from 0 to 1. When the clk is 1, a ff is able to change.




In this design, the bubble before the clk are deleted.
 
# Asynchronous up-down counter



- We have already considered up-counters and down-counters separately.
- But both of the units can be combined in a single *up-down counter*.
  - Such a counter is also called a *multimode counter*.




# Synchronous counters

- The ripple or asynchronous counter is the simplest to build, but its highest operating frequency is **limited because of ripple action**.
  - Each flip-flop has a delay time.
  - In ripple counters these delay times are additive and the total “settling” time for the counter is approximately the product of the delay time of a single flip-flop and the total number of flip-flops.
  - There is the possibility of glitches occurring at the output of decoding gates used with a ripple counter.
- Both of these problems can be overcome, if all the flip-flops are clocked synchronously.
- The resulting circuit is known as a *synchronous counter*.
 
# Synchronous counters


- Synchronous counter with parallel carry.*





 
# Synchronous counters

- *Synchronous counter with ripple carry.*
  - As the number of stages increases, the number of AND gates also increases, along with the number of inputs for each of those AND gates.


 
# Synchronous down-counter


- A parallel down-counter can be made to count down by using the inverted outputs of flip-flops to feed the various logic gates.


 
# Synchronous up-down counter




- Combining both the functions of up- and down-counting in a single counter, we can make a *synchronous up-down counter*.



 
# Design a synchronous counter

- Following certain general steps, synchronous counters of any given count sequence and modulus can be designed. The steps are listed below:
  - From the given word description of the problem, draw a state diagram that describes the operation of the counter.
  - From the state table, write the **count sequences** in the form of a table.
  - Find the **number** of flip-flops required.
  - Decide the **type of flip-flop** to be used for the design of the counter. Then determine the **flip-flop inputs** that must be present for the desired next state from the present state using the excitation table of the flip-flops.
  - Prepare **K-maps for each flip-flop input** in terms of flip-flop outputs as the input variables. Simplify the K-maps and obtain the minimized expressions.
  - Connect the circuit using flip-flops and other gates corresponding to the minimized expressions.



# Design a MOD-5 counter

 

# Design a MOD-5 counter



*the ff type can be NOT just JK.*

Present			Next			Flip-flop Inputs					
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$J_{A2}$	$K_{A2}$	$J_{A1}$	$K_{A1}$	$J_{A0}$	$K_{A0}$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	0	0	0	X	1	0	X	0	X

# Design a MOD-5 counter



$A_2 \backslash A_1 A_0$	00	01	11	10
0			1	
1	X	X	X	X

$$J_{A2} = A_1 A_0$$

$A_2 \backslash A_1 A_0$	00	01	11	10
0		1	X	X
1		X	X	X

$$J_{A1} = A_0$$

$A_2 \backslash A_1 A_0$	00	01	11	10
0	1	X	X	1
1		X	X	X

$$J_{A0} = A_2'$$

$A_2 \backslash A_1 A_0$	00	01	11	10
0	X	X	X	X
1	1	X	X	X

$$K_{A2} = 1$$

$A_2 \backslash A_1 A_0$	00	01	11	10
0	X	X	1	
1	X	X	X	X

$$K_{A1} = A_0$$


$A_2 \backslash A_1 A_0$	00	01	11	10
0	X	1	1	X
1	X	X	X	X

$$K_{A0} = 1$$


 
# Lock out

- In the counters with modulus less than  $2^n$ , it may happen that the counter by chance finds itself in any one of the unused states.
- If by chance the counter enters into any one of these unused states, its next state will not be known.
- It may be possible that the counter might go from one unused state to another and never arrive at a used state.
- A counter whose unused states have this feature is said to suffer from *lock out*.
- To ensure that lock out does not occur, we design the counter **assuming the next state to be the initial state, from each of the unused states**.



The solution is connect each invalid state to a valid one. It is recommended to reduce the different digit of the 2 state.

Counters

So in the state table, row of invalid state should be written as well.