

Latches and Flip-flops

CS207 Chapter 6

James YU

yujq3@sustech.edu.cn

Department of Computer Science and Engineering
Southern University of Science and Technology

Oct. 26, 2022



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY

Sequential logic


- Logic circuits for digital systems:
 - combinational logic (previous lectures),
 - sequential logic.
- Combinational?
 - Output determined by the combination of inputs.
 - Perform an operation specified by a set (combination) of Boolean functions.

Sequential logic

- Almost all electronic consumer products
 - send, receive, store, retrieve, and process information
 - depends on the ability to store binary – has memory.
- Sequential circuits
 - act as storage elements.
- The logic circuits whose ^②outputs at any instant of time depend on the ^①**present inputs** as well as on the **past outputs** are called *sequential circuits*.
stored

Sequential logic

- ② The logic circuits whose outputs at any instant of time depend on the **present inputs** as well as on the **past outputs** are called *sequential circuits*.
- A combinational circuit, but with
 - memory elements connected in a feedback path.
 - Outputs are binary functions of not only inputs, but also the present state of the circuit.
 - A **memory element** is a medium in which one bit of information (0 or 1) can be stored or retained until necessary, and thereafter its contents can be replaced by a new value.

 



Sequential logic

time-related → fundamental

- Sequential circuits are broadly classified into two main categories, known as
 - ① **synchronous** or **clocked sequential circuits**, and *change at the SAME time*
 - ② **asynchronous** or **unclocked sequential circuits**,
- depending on the timing of their signals.
- ① • A sequential circuit whose behavior can be defined from **the knowledge of its signal at discrete instants of time** is referred to as a **synchronous sequential circuit**.
 - The synchronization is achieved by a timing device known as a **system clock**.
 - The outputs are affected **only** with the application of a clock pulse.
- ② • A sequential circuit whose behavior **depends upon the sequence in which the input signals change** is referred to as an **asynchronous sequential circuit**.

Sequential logic


- A sequential circuit whose behavior can be defined from **the knowledge of its signal at discrete instants of time** is referred to as a **synchronous sequential circuit**.
 - The synchronization is achieved by a timing device known as a system clock.
 - The outputs are affected only with the application of a clock pulse.
- Clock pulse: when changes will happen; Other signals: what changes will happen.
- Clocked sequential circuits:
 - Synchronous sequential circuits that use clock to control.
 - Synchronous because the circuit activity and the updating of storage are synchronized.
cause to occur or operate
at the same time or rate

Sequential logic



- Memory element: *physical equipment* flip-flop.

 - A binary storage device storing one bit;
- Change in state happens **only** during clock pulse transition;
- Loop cut when clock is inactive, no update.



clock signal frequency \updownarrow




Flip-flops



- It can have only two states, either the 1 state or the 0 state. *store 1 bit information*
- The general block diagram representation of a flip-flop is shown below:
 - It has one or more inputs and two outputs.
 - The two outputs are complementary to each other.

$Q=1, Q'=0$
 $Q=0, Q'=1$

 

$Q \leftrightarrow f$
output of mux
↓
internal stage


- Normally, the state of Q is called the **state** of the flip-flop, whereas the state of Q' is called the **complementary state** of the flip-flop.
combining in such a way
as to enhance or
emphasize the qualities of
each other or another

Flip-flops *apply to latch*



- There has always been considerable confusion over the use of the terms *latch* and *flip-flop*.
 - A *flip-flop* is a device which changes its state at times when a change is taking place in the clock signal.
 - An *asynchronous latch* is continuously monitoring the input signals and changes its state at times when an input signal is changing.
 - A *synchronous latch* is continuously monitoring the input signals, but only can changes its state when a control signal is active.

 a circuit that retains whatever output state results from a momentary input signal until reset by another signal.



flip-flop is an edge-triggered type of memory circuit while the latch is a level-triggered type. It means that the output of a latch changes whenever the input changes. On the other hand, the latch only changes its state whenever the control signal goes from low to high and high to low.

A flip-flop is a digital memory circuit that stores one bit of data. They are the primary blocks of the most sequential circuits. It is also called one-bit memory, binary, or a bistable multivibrator. Flip-flops act as memory elements in a sequential circuit. You can obtain the output in the sequential circuits using a flip-flop, a combinational circuit, or both.

A flip-flop state repeatedly changes at an active state of the clock pulses. They remain unaffected even when the clock pulse does not stay active. The clocked flip-flops particularly act as the memory elements of the synchronous sequential circuit- while the un-clocked ones (latches) function as the memory elements of asynchronous sequential circuits.

There are mainly four types of flip-flops:


- JK Flip-Flop
- SR (Set-Reset) Flip-Flop
- Data or Delay (D) Flip-Flop
- Toggle (T) Flip-Flop

A latch is an electronic device that changes its output immediately on the basis of the applied input. One can use it to store either 0 or 1 at a specified time. A latch contains two inputs- SET and RESET, and it also has two outputs. They complement each other. One can use a latch for storing one bit of data. It is a memory device- just like the flip-flop. But it is not synchronous, and it does not work on the edges of the clock like the flip-flop.



SR latches

 - By cross coupling a pair of NOR gates, we have a first latch: **SR latch**.
 - The set and reset inputs are labelled *S* and *R* respectively.



start from left to right
to go through all lines

- The **state table** of SR latch is shown below

truth table

reset
(to 0)

set
(to 1)

	Present		Next	
	S_t	R_t	Q_t	Q_{t+1}
	0	0	0	0
	0	0	1	1
	0	1	0	0
	0	1	1	0
	1	0	0	1
	1	0	1	1
	1	1	Forbidden	

we use subscript
 t to represent current time

→ head row

$S=R=0$
⇒ NOT to change Q


Sometimes $Q_t = Q'_t = 1$

SR latches

NAND gates is MOSTLY used in manufacturing





- From the k-map: $Q_{t+1} = S + R'Q$.

 

based on or in accordance
with what is generally done
or believed:

S \ RQ	00	01	11	10
		1		
0		1	X	X
1	1	1	X	X

- A more conventional form:

  

2/1 level
S/R on the top
NAND/NOR gate

Controlled SR latch


$$\text{NAND} \begin{cases} 0 & I_1 = I_2 = 1 \\ 1 & \text{otherwise} \end{cases}$$



- The transparency of SR latches can be controlled by an additional signal G :

- If $G = 0$, the outputs of first-level NAND gates are always 1, disabling any changes in the second level gates.
- If G makes a transition from 0 to 1, the first-level NAND gates are enabled, making the latch active.
 
$$\begin{aligned} (0 \cdot 1)' &= 1 \\ (1 \cdot 1)' &= 0 \end{aligned}$$



- A problem with SR latches: **state is indeterminate when S and R are both 1.**
 \Rightarrow controlled D latch




Controlled D latch

the state when $S=R=1$
can't determine
(controlled) SR gates

- D latch is designed to handle this problem.
 - Also called **transparent latch**, D for data.
 - Ensure the previous S and R are never equal to 1 at the same time.

$$D=0 \Rightarrow Q=0$$

$$D=1 \Rightarrow Q=1$$

 

enable line
 $G=0 \Rightarrow$ disable
Q will NOT
response
D will NOT
be reflected

complementary
 $S=0$
 $R=1$
 $S=1$
 $R=0$
 $S=R$ is IMpossible

Present		Next
D_t	Q_t	Q_{t+1}
0	0	0
0	1	0
1	0	1
1	1	1

Controlled D latch

called transparent latch $\Leftarrow \begin{cases} 1 \rightarrow 1 \\ 0 \rightarrow 1 \end{cases}$






- The controlled D latch has the advantage that it only requires one data input and there is no input condition that has to be avoided. *SR latch needs to forbidden 11*
- Transparent?
 - Data input is transferred to Q output **when enable is asserted**. The output follows the input.
state a fact or belief confidently and forcefully
 - When enable is de-asserted, the information is stored.

Latches

block diagram



   南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY




Q prime or
Q bar is
both okay

Flip-flops *invited based on latches*



 
- Latch or flip-flop state change by a control input.
 - The event is called **trigger**.
- When latches are memories, difficulty arises:
 - State changes as soon as clock switches to 1.
 - Infinite loop during clock-1.



JK flip-flop



 - Latch circuits are **not** suitable for operation in synchronous sequential circuits because of their transparency.
 - Flip-flops are used as the basic memory elements, which only respond to a transition on a clock input.
 - A typical example is called JK flip-flop (JKFF).



Negative-edge-triggered.



Present			Next
J_t	K_t	Q_t	Q_{t+1}
0	0	0	0
	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$J = K = 0$
 Q retain

JK flip-flop



  - J is S , and K is R .
- When $J = K = 1$, the flip-flop **toggles**.
switch from one effect, feature, or state to another by using a toggle
- Combining the two AND gates with the SR latch circuit, we have the following reduced circuit:




- However, the above circuit alone still cannot resolve the problem with latches.
 - A master-slave JKFF can be used.

JK flip-flop



 - The master-slave JKFF consists of two SR latches, the master and the slave.
 - The master is clocked in the normal way, while the slave clock is **inverted**:




- When the clock is 1, the **master latch** works transparently.
 - However, as the slave latch is disabled at the same time, **no** changes will be reflected on the output.

JK flip-flop



The D ff is consist of 2 D

 - The master-slave JKFF consists of two SR latches, the master and the slave.
 - The master is clocked in the normal way, while the slave clock is inverted:



- Upon the clock is changed to 0, the slave is activated to reflect the data from master to the output.
 - However, the master latch is disabled: no further changes on input will be reflected.

Asynchronous control



unlocked sequential

- As well as the J , K , and clock inputs, a master-slave JKFF may also have one or two additional controls to set the state of flip-flop irrespective of clock:
 - These asynchronous controls are usually called *preset* and *clear*.

(of two or more objects or events) not existing or happening at the same time.


<i>clear</i> Cl	<i>pre set</i> Pr	Q
1	1	Forbidden
1	0	0
0	1	1
0	0	X

- If $Cl = 1$ and $Pr = 0$ both master and slave are cleared to 0.
- If $Cl = 0$ and $Pr = 1$ the flip-flop is preset to 1.
- Active high on Cl and Pr will override J and K .

Asynchronous control



 南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY





D flip-flop


data



  - A negative edge triggered D type master-slave FF consists of a pair of D latches:




 - Right is the symbolic diagram of DFF.
- The triangle is termed *dynamic input indicator*.





D flip-flop

 - An alternative configuration of a DFF consists of three pairs of cross-coupled NAND gates, each pair constituting a basic S'R' latch:



- The latch is stable when $S' = R' = 1, Q = 0$.
- To change the state, S' must make a $1 \rightarrow 0$ transition.



D flip-flop

  

JK flip-flop revisit



 
 
- The previous DFF can be modified to provide the function of a JKFF as follows:




- If $J = K = 1$ and $Q' = 1$, the input to DFF is 1, the Q outputs 1.
- Think what happens when $J = 1$ and $K = 0$, and vice versa.

T flip-flop

  - Finally, a T flip-flop toggles the state when input $T = 1$ upon clock signal.
- It is simple to construct a TFF from JKFF:



- or DFF:

 

Characteristic table

- A *characteristic table* describes the logical properties of a flip-flop by describing its operation in tabular form.

J	K	Q_{t+1}	
0	0	Q_t	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'_t	Complement

D	Q_{t+1}	
0	0	Reset
1	1	Set

T	Q_{t+1}	
0	Q_t	No change
1	Q'_t	Complement

Characteristic equation



- A characteristic equation describes the logical properties of a flip-flop by describing its Boolean function.

In some characteristic equations, the j and k and other input may be represent by other variables, but when calculate the equations, do not forget to remove the parenthesis

- DFF: $Q_{t+1} = D$.
- JKFF: $Q_{t+1} = JQ'_t + K'Q_t$.
- TFF: $Q_{t+1} = T \oplus Q_t$.

D Q_{t+1}		
0	0	Reset
1	1	Set

J	K	Q_{t+1}	
0	0	Q_t	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'_t	Complement

T	Q_{t+1}	
0	Q_t	No change
1	Q'_t	Complement