

# Digital Logic Assignment 3

12111448 Hou Fangmin

## t1

A PN flipflop has four operations: clear to 0, no change, complement, and set to 1, when inputs P and N are 00, 01, 10, and 11, respectively.

### 1


Tabulate the characteristic table

$P$	$N$	$Q_{t+1}$	
0	0	0	clear to 0
0	1	$Q_t$	no change
1	0	$Q'_t$	complement
1	1	1	set to 1
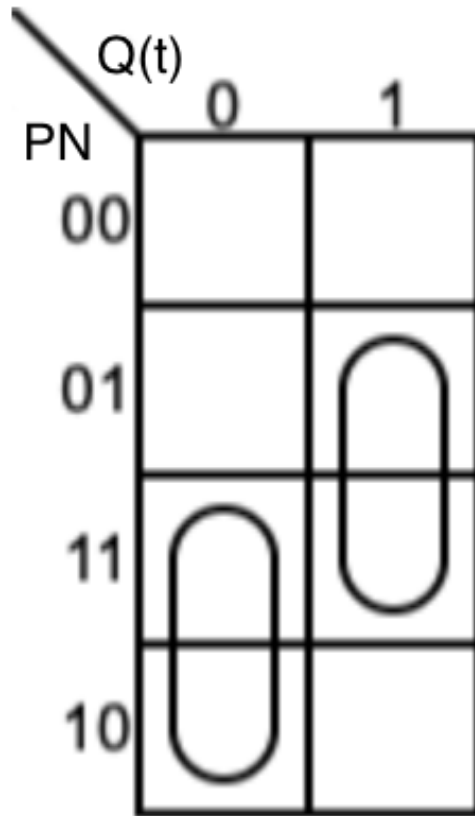
### 2

Derive the characteristic equation

Fron the above characteristic table we can get the K map,



Then we can get the characteristic equation:

$$Q_{t+1} = P Q'_t + N Q_t \tag{1}$$


### 3

Tabulate the excitation table

$Q(t)$	$Q(t + 1)$	$P$	$N$
0	0	0	$X$
0	1	1	$X$
1	0	$X$	0
1	1	$X$	1
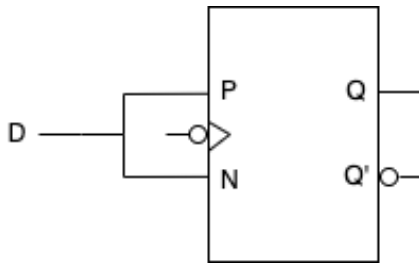
### 4

Show how the PN flipflop can be converted to a D flipflop



For D flipflop, when D=0, Q(t+1)=0; D=1, Q(t+1)=1.

To convert a PN flipflop to a D flipflop, just let P and N connect to one input D before the PN flipflop, then when D=1, P=N=1, Q=1; when D=0, P=N=0, Q=0; which is the same as the output of D flipflop.

## t2

(20 points) A sequential circuit has two JK flip-flops A and B and one input x. The circuit is described by the following flip-flop input equations:  $J_A = x'$ ,  $K_A = B$ ,  $J_B = x$ ,  $K_B = A'$ .

### 1

Derive the state equations A(t + 1) and B(t + 1) by substituting the input equations for the J and K variables. raw the state diagram of the circuit.

For JF flipflop,


$$Q_{t+1} = JQ'_t + K'Q_t \tag{2}$$

then

$$A(t + 1) = JA' + K'A = x'A' + B'A \tag{3}$$

$$B(t + 1) = xB' + AB \tag{4}$$

present	present	input	next	next
A(t)	B(t)	x	A(t+1)	B(t+1)
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

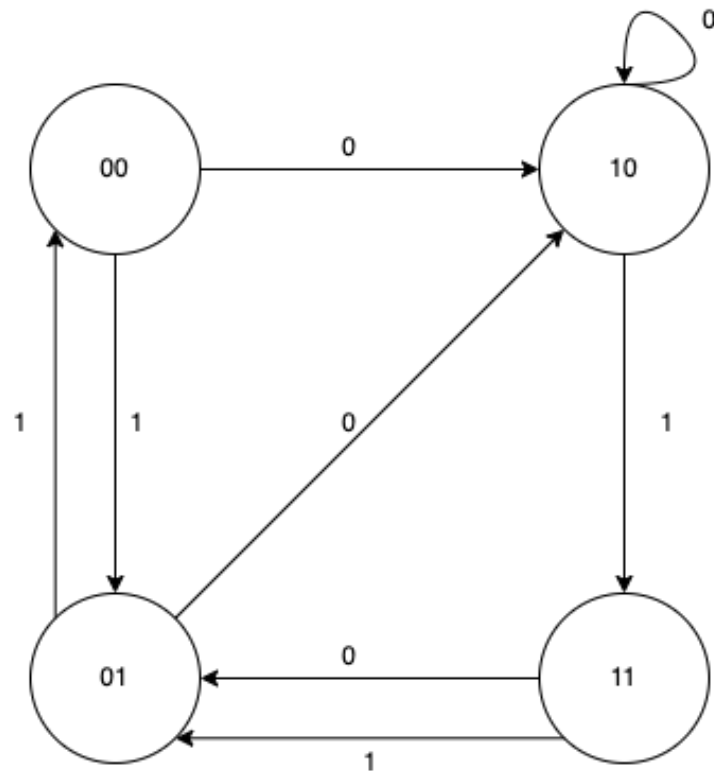


### t3

(20 points) A sequential circuit has two JK flipflops A and B, two inputs x and y, and one output z. The flipflop input equations and circuit output equation are  $JA = Bx' + B'y$ ,  $KA = Bx' + y'$ ,  $JB = Ax'$ ,  $KB = A + xy'$ ,  $z = Axy + Bx'y'$ .

### 1

Draw the logic diagram of the circuit.

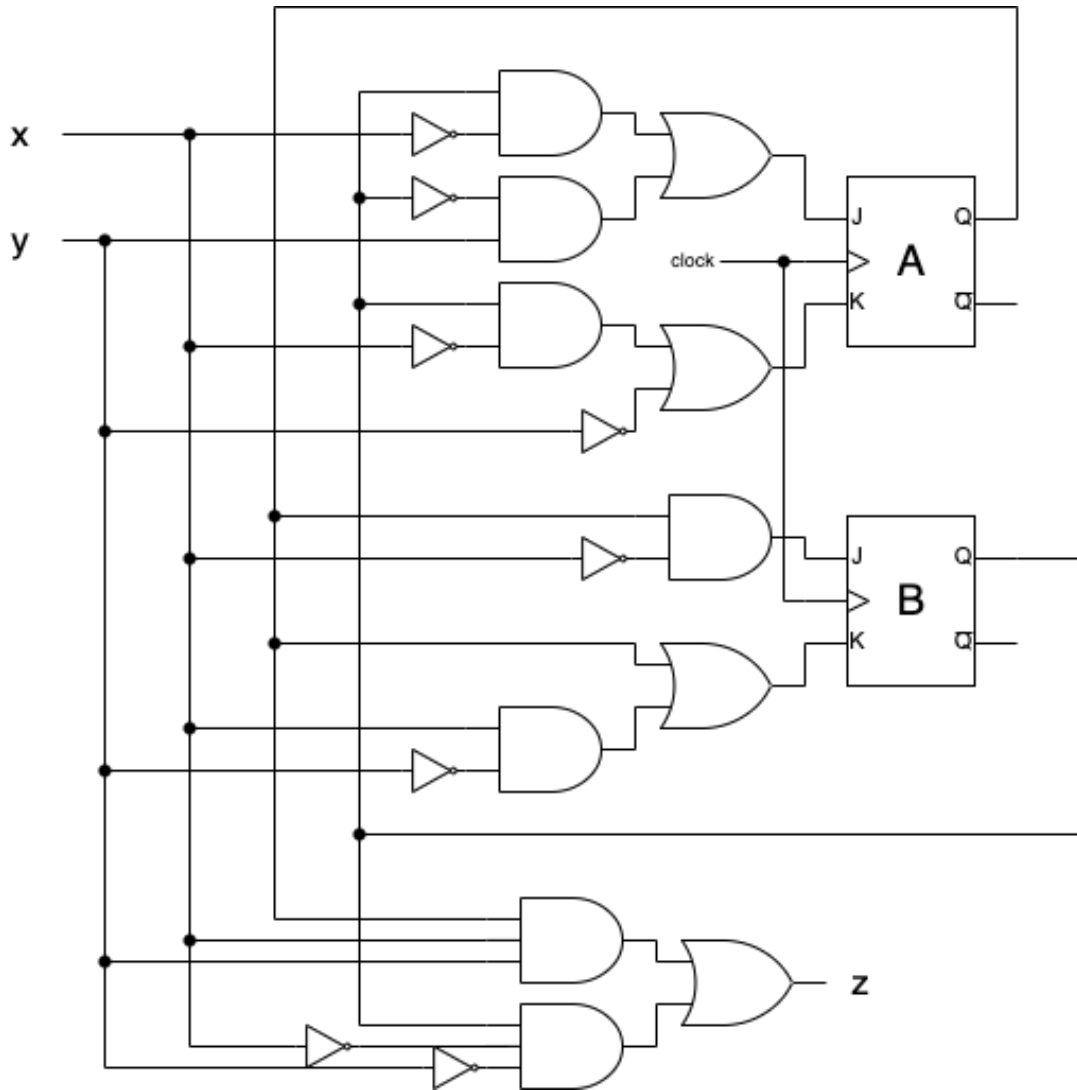

2

Tabulate the state table.

As for JK flip flop,


$$Q(t+1) = JQ' + K'Q \quad (5)$$

then

$$A(t+1) = (Bx' + B'y)A' + (Bx' + y')A \quad (6)$$

$$B(t+1) = (Ax')B' + (A + xy')B \quad (7)$$

present	present	input	input	next	next	output
A	B	x	y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	1	0	0
0	1	0	0	1	1	1
0	1	0	1	1	1	0
0	1	1	0	0	0	0
0	1	1	1	0	1	0
1	0	0	0	0	1	0
1	0	0	1	1	1	0
1	0	1	0	0	0	0
1	0	1	1	1	0	1
1	1	0	0	0	0	1
1	1	0	1	0	0	0
1	1	1	0	0	0	0
1	1	1	1	1	0	1

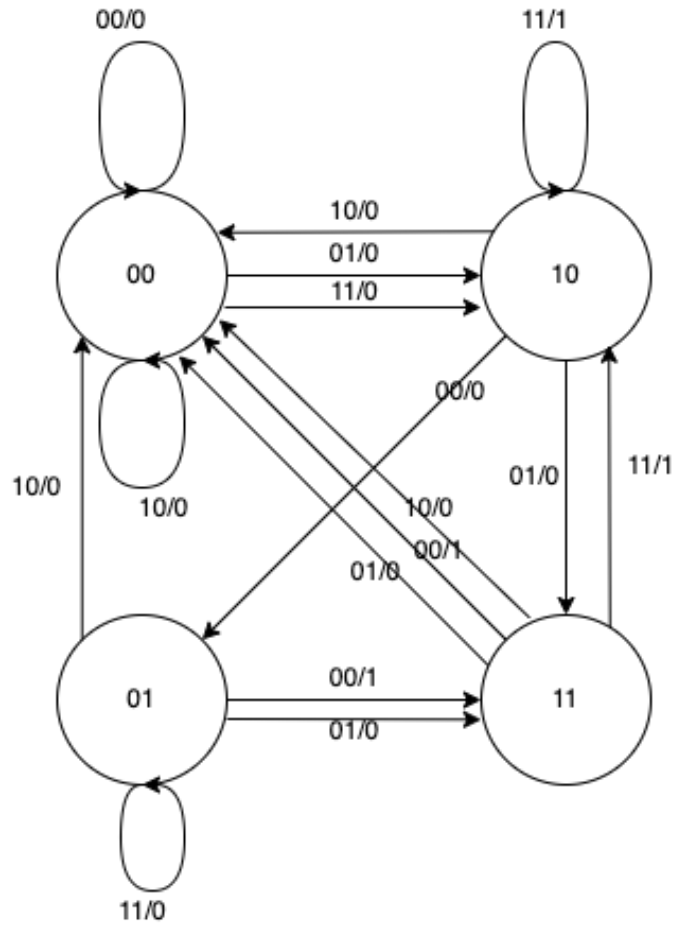

### 3

Derive the state equations for A and B.

As for JK flip flop,

$$Q(t+1) = JQ' + K'Q \quad (8)$$

then

$$A(t+1) = (Bx' + B'y)A' + (Bx' + y')'A = A'Bx' + B'y + Axy \quad (9)$$

$$B(t+1) = (Ax')B' + (A + xy')'B = AB'x' + A'Bx' + A'By \quad (10)$$

### t4


(20 points) For the following state table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

1

Draw the corresponding state diagram.



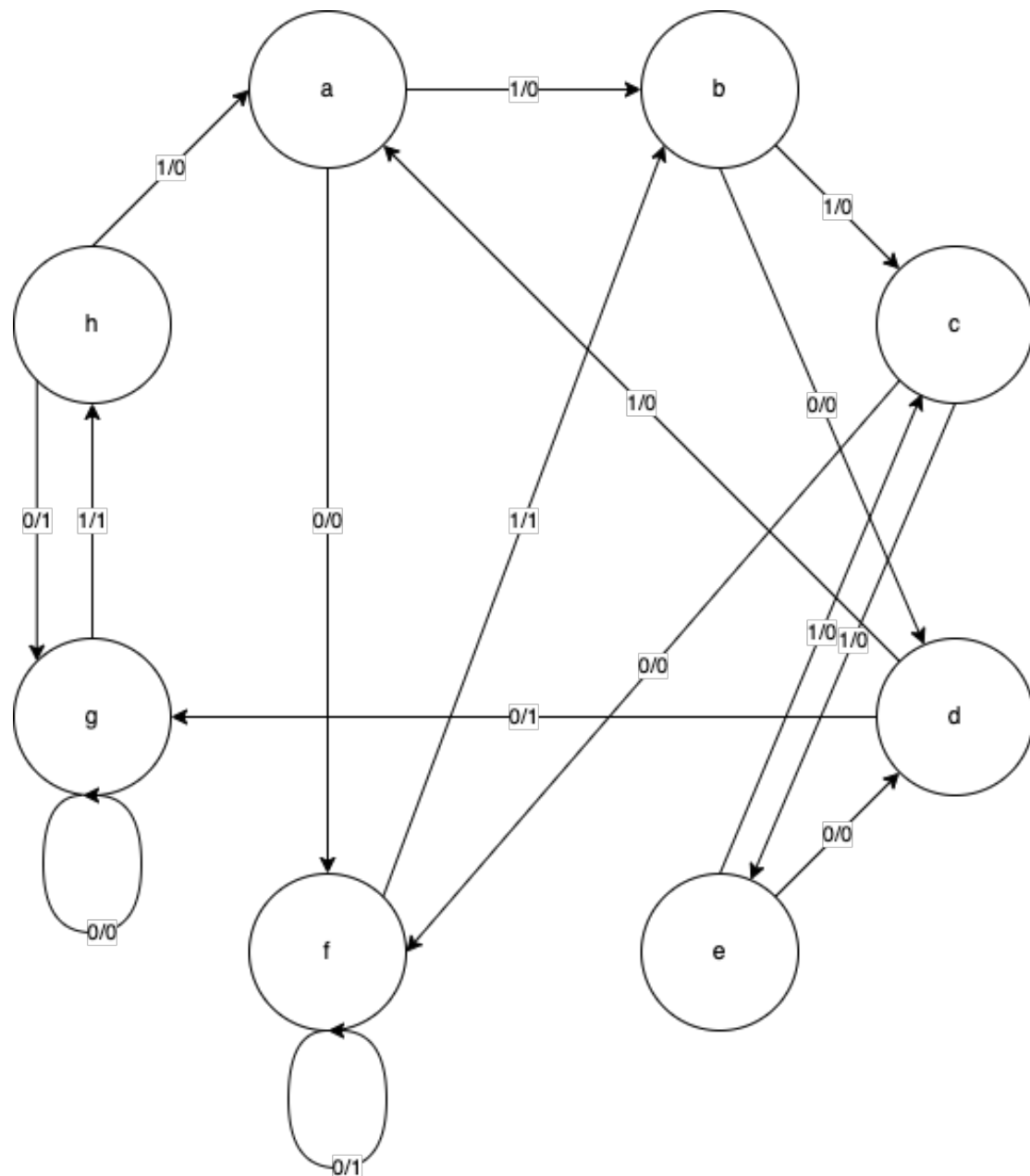

## 2

Tabulate the reduced state table.

When the present state is e or b, other elements in the row are the same, so the e row is deleted, and e is replaced by b.

And for the same reason, h can be replaced by d.


After replacing e by b, the c row and a row become similar, and c is replaced by a.

Then we get the table below:

present state	Next state	next state	output	output
	x=0	x=1	x=0	x=1
a	f	b	0	0
b	d	a	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

3

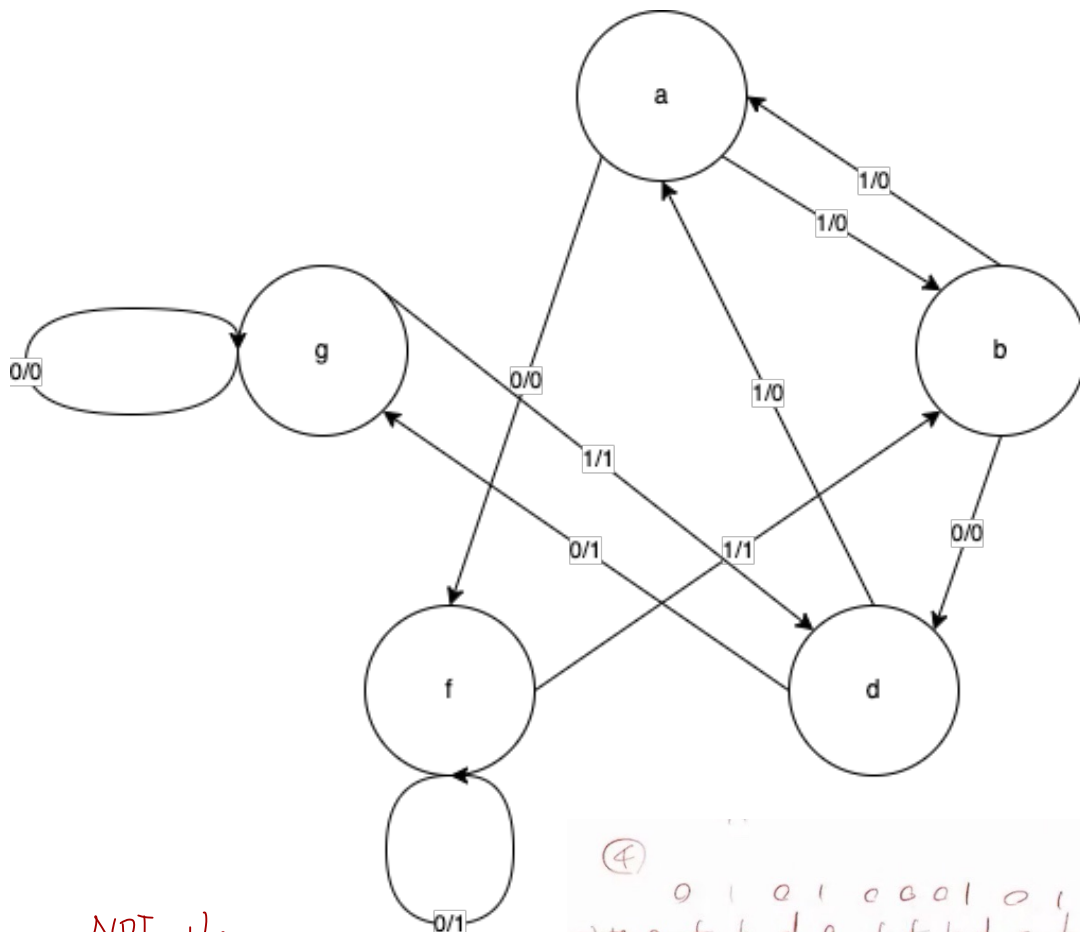Draw the state diagram corresponding to the reduced state table.



4

NOT the state sequence  
the OUTPUT sequence  
what we need is

④  
0 1 0 1 0 0 1 0 1 1 1  
state a f b d a f f b d a b d  
output 0 1 0 0 0 1 1 0 0 0 0

Determine the output sequence for input sequence 01010010111 (from left to right) with the original state table and the reduced state table, starting from a.

- Original: a--f(0)--b(1)--d(0)--a(0)--f(0)--f(1)--b(1)--d(0)--a(0)--b(0)--c(0)
- Reduced: a--f(0)--b(1)--d(0)--a(0)--f(0)--f(1)--b(1)--d(0)--a(0)--b(0)--a(0)

t5

(20 points) Obtain the simplified input equations for a sequential circuit that uses T flip-flops and is specified by the state diagram below. To obtain the input  $\{0 : \text{no change}$


$\begin{cases} 0 : \text{no change} \\ 1 : \text{complement} \end{cases}$

- ① draw state table with input of ff added on it.  
input of ff can be obtained from excitation table
- ② use state and input of circuit draw k map of every input of ff.


Let  $x$  be the input, the state of A and B be the state of 2 T flip flops.

present	present	input	next	next	T flip flop	T flip flop
A	B	x	A	B	$T_A$	$T_B$
0	0	0	0	1	0	1
0	0	1	0	0	0	0
0	1	0	1	1	1	0
0	1	1	1	0	1	1
1	0	0	1	1	0	1
1	0	1	1	0	0	0
1	1	0	0	0	1	1
1	1	1	1	1	0	0

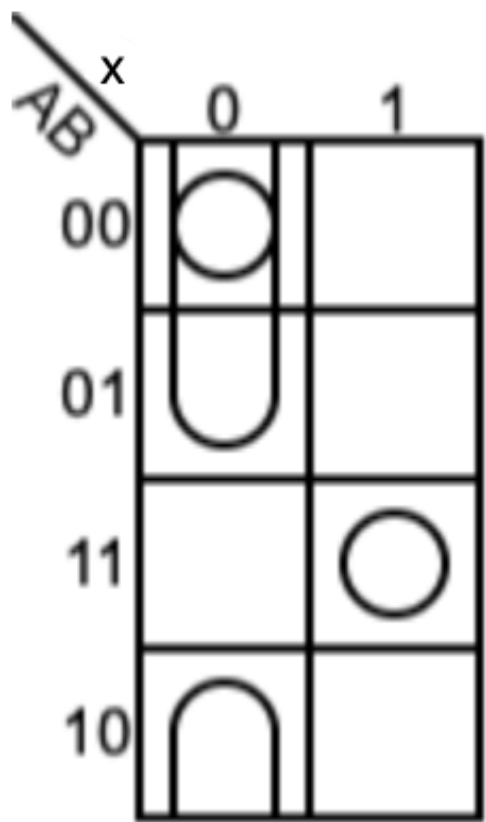
Then we get the K map of  $A, B, T_A, T_B$





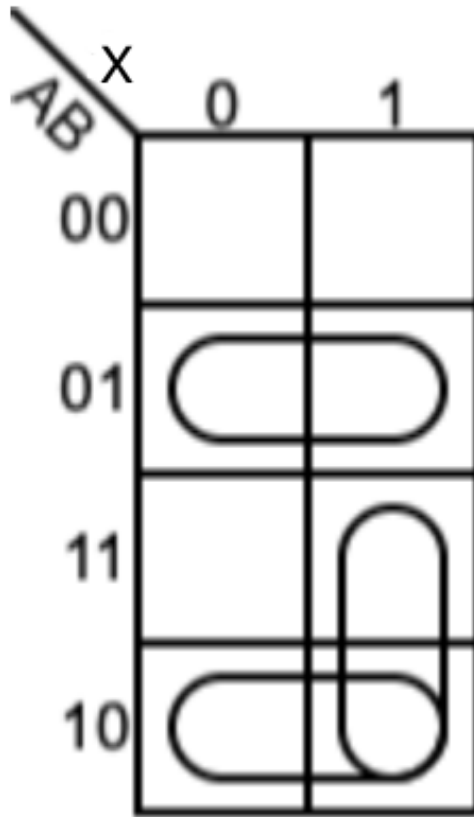

$$A_{t+1} = A'B + AB' + Ax$$
(11)

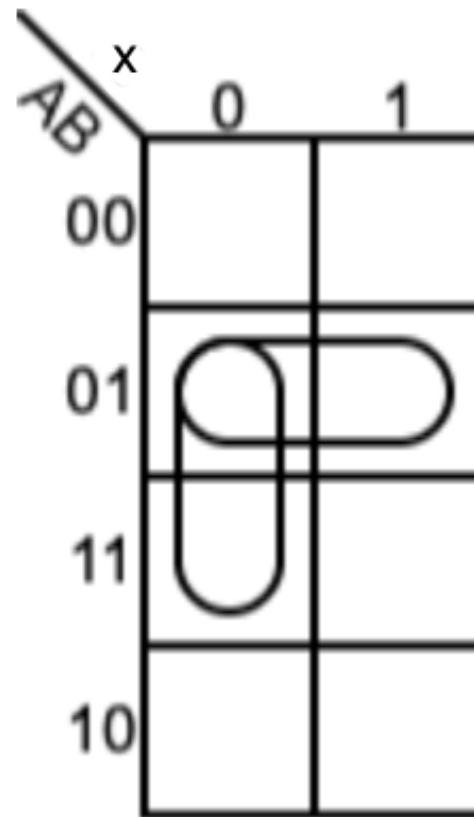

$$B_{t+1} = A'x' + B'x' + ABx \quad (12)$$



$$T_A = Bx' + A'B \quad (13)$$

AB \ x		0	1
00			
01			
11			
10			

$$T_B = Ax' + B'x' + A'Bx \quad (14)$$