

Gate-level Minimization

CS207 Chapter 3

James YU

yujq3@sustech.edu.cn

Department of Computer Science and Engineering
Southern University of Science and Technology

Sept. 21, 2022



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY

Gate-level minimization

task is find optimal



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY

- The complexity of digital logic gates to implement a Boolean function is directly related to the complexity of algebraic expression.
- Gate-level minimization is the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.
 - Difficult by hand for more than few inputs.
 - Typically by computer, need to understand the underlying principle.

Can only solve up to 4 variable
other by EDA tool.

Electronic design automation

But the principle is same

The map method

also called gate-level minimization



put forward (an idea or plan) for consideration or discussion by others

- The map method, first proposed by Veitch and slightly improvised by Karnaugh, provides a simple, straightforward procedure for the simplification of Boolean functions.
 - Called *Karnaugh map*. *k map*
- The map is a diagram consisting of *squares*. For n variables on a Karnaugh map there are 2^n numbers of squares.
 - Each square or cell represents one of the minterms.
 - Since any Boolean function can be expressed as a sum of minterms, it is possible to recognize a Boolean function graphically in the map from the area enclosed by those squares whose minterms appear in the function.

based on minterm & maxterm

- 1 Select K-map according to the number of variables.
- 2 Identify minterms or maxterms as given in problem.
- 3 For SOP put 1's in blocks of K-map respective to the minterms (0's elsewhere).
- 4 For POS put 0's in blocks of K-map respective to the maxterms (1's elsewhere).
- 5 Make rectangular groups containing total terms in power of two like 2,4,8 ..(except 1) and try to cover as many elements as you can in one group.
- 6 From the groups made in step 5 find the product terms and sum them up for SOP form

Two-variable K-map

- A two-variable system can form four minterms

one and only one input to produce
refer to a term that has

small squares
(cells)

注意 K-map 画法.

	0	1
0	m_0	m_1
1	m_2	m_3

	0	1
0	$A'B'$	$A'B$
1	AB'	AB

	0	1
0	0	1
1	1	1

- The two-variable Karnaugh map is a useful way to represent any of the 16 Boolean functions.

- Example:

unique minterm table

$$\begin{aligned}
 A + B &= A(\overline{B} + B) + B(\overline{A} + A) \\
 &= AB + AB' + AB + A'B = AB + AB' + A'B
 \end{aligned}$$

add $(x+x')$ for missing term x
label minterm appear at this place

- So the squares corresponding to AB , AB' , and $A'B$ are marked with 1. other 0.

Three-variable K-map



- Since there are eight minterms for three variables, the map consists of eight cells or squares.
 - Minterms are arranged, not according to the binary sequence, but according to the sequence similar to the gray code.
 - **Between two consecutive rows or columns, only one single variable changes its logic value from 0 to 1 or from 1 to 0.**

BC		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

the first & last column is adjacent too
adjacent column

only 1 bit is changed

||
principle of K map

unique K map of 3 variables

$$(5)_{10} = (101)_2$$

↓ ↓ ↓
A B C

in 2 variable case
there's no need to
consider adjacent

Three-variable K-map



- To understand the usefulness of the map for simplifying the Boolean functions, we must observe the basic properties of the adjacent squares.
 - Any two adjacent squares in the Karnaugh map differ by only one variable, which is complemented in one square and uncomplemented in one of the adjacent squares.
 - The sum of two minterms can be simplified to a single AND term consisting of less number of literals.
 - $m_1 + m_5 = A'B'C + AB'C = (A' + A)B'C = B'C$

row & column
BOTH adjacent

$(101)_2 = (5)_{10}$


		BC			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

adjacent in k map
 \Rightarrow CAN simplification

Three-variable K-map



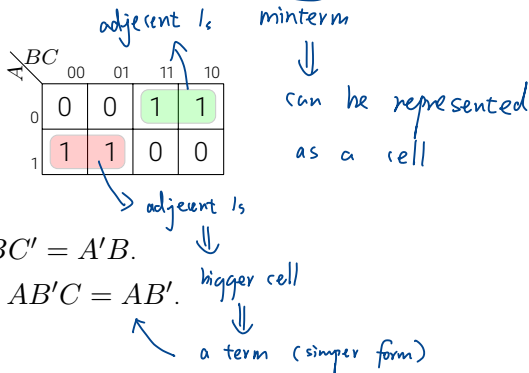- Example: Simplify the Boolean function $F = \underline{A'BC} + A'BC' + AB'C' + AB'C$.



- The first row: $A'BC + A'BC' = A'B$.
- The second row: $AB'C' + AB'C = AB'$.
- $F = A'B + AB'$.

Three-variable K-map



- Example: Simplify the Boolean function $F = A'BC + AB'C' + ABC + ABC'$.

$A \backslash BC$	00	01	11	10
0	0	0	1	0
1	1	0	1	1



how to
create
adjacent

try to group
every term

- The third column: $A'BC + ABC = BC$.
- The second row: $AB'C' + ABC' = AC'$.
- $F = BC + AC'$.

fixed value (1 \Rightarrow x 0 \Rightarrow x)
in group!

Three-variable K-map



- Example: Simplify the Boolean function $F = \sum(1, 2, 3, 5, 7)$.

$A \backslash BC$	00	01	11	10
0	0	1	1	1
1	0	1	1	0

1 can be reused

Don't forget the SKIP!

- $F = C + A'B$.

① square can be represented by one literal

② group can be different from 2 cells

Why the "1" in cells can be reused?

- As adjacent cells differs only by one variable, it can be group, and the group can be represented by the literals that do not changed.
Because for SOP, $A + A' = 1$, the $A'BC + ABC = BC$.
- And for repeat, $A + A = A$.

$$\text{So } A'BC + AB'C + ABC$$

$$= A'BC + AB'C + \underbrace{ABC + ABC}$$

$$= BC + AC$$

Three-variable K-map

- Example: Simplify the Boolean function $F = \sum(0, 2, 4, 5, 6)$.

$\backslash BC$	00	01	11	10
0	1	0	0	1
1	1	1	0	1


Don't forget the
adjacent between
the first & last
columns.

- $F = C' + AB'$.

Four-variable K-map

There have European K-map as well.
we introduce the US K-map

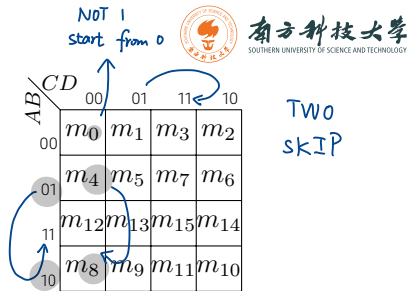
- Similar to the method used for two-variable and three-variable Karnaugh maps, four-variable Karnaugh maps may be constructed with 16 squares consisting of 16 minterms.



Four-variable K-map

- Two, four, or eight adjacent squares can be combined to reduce the number of literals in a function.
- The squares of the top and bottom rows as well as leftmost and rightmost columns may be combined.
 - When two adjacent squares are combined, it is called a *pair* and represents a term with three literals.
 - Four adjacent squares, when combined, are called a *quad* and its number of literals is two.
 - If eight adjacent squares are combined, it is called an *octet* and represents a term with one literal.
 - If, in the case all sixteen squares can be combined, the function will be reduced to

1.

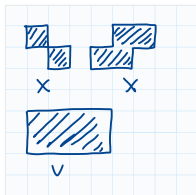

Four-variable K-map

ALWAYS

& minimize } \Rightarrow use K-map

\Rightarrow 4 variables K-map
the max index is 15
 \uparrow



- Example: Simplify the Boolean function
 $F = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$.

- $A'B'C'D + A'BC'D = A'C'D$,
- $ABC'D' + ABC'D = ABC'$,
- $F = A'C'D + ABC' + ACD + AB'C$.
- This reduced expression is not a unique one.
- If pairs are formed in different ways, the simplified expression will be different.

\Rightarrow compare with next page's
K-map

AB \ CD	00	01	11	10
00		1		
01		1		
11	1	1	1	
10			1	1

Four-variable K-map



- Example: Simplify the Boolean function
 $F = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$.
- $F = A'C'D + ABC' + ABD + AB'C$.

AB \ CD	CD			
	00	01	11	10
00		1		
01		1		
11	1	1	1	
10			1	1

AB \ CD	CD			
	00	01	11	10
00		1		
01		1		
11	1	1	1	
10			1	1

Four-variable K-map



- Example: Simplify the Boolean function
 $F = \sum(7, 9, 10, 11, 12, 13, 14, 15)$.
- $F = AB + AC + AD + BCD$.

AB \ CD	00	01	11	10
00				
01			1	
11	1	1	1	1
10		1	1	1

NOT let it
be alone. it
can be
connected to
other

Four-variable K-map



- Example: Plot the logical expression
make a schematic or technical drawing of that shows how things work or how they are constructed
 $F(A, B, C, D) =$

$$F(A, B, C, D) =$$

$ABCD + AB'C'D' + AB'C + AB$ on a
four-variable Karnaugh map.

AB \ CD	00	01	11	10
00				
01				
11	1	1	1	1
10	1		1	1

$$\begin{aligned} &F(A, B, C, D) \\ &= ABCD + AB'C'D' + AB'C + AB \\ &= ABCD + AB'C'D' + AB'C(D + D') \\ &\quad + AB(C + C')(D + D') \\ &= \dots \\ &= \sum(8, 10, 11, 12, 13, 14, 15) \\ &= AB + AC + AD' \end{aligned}$$

this step can be left out.
we can just use this to fill 1 in
k-map

Four-variable K-map



- Simplify the expression $F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$.

AB \ CD	CD			
	00	01	11	10
00	1	1		1
01	1	1		1
11	1	1		1
10	1	1		

Four-variable K-map



- Simplify the expression $F(A, B, C, D) = A'B'C' + B'CD' + A'BCD' + AB'C'$.

$$\begin{aligned} & F(A, B, C, D) \\ &= A'B'C'(D + D') + B'CD'(A + A') \\ &\quad + A'BCD' + AB'C'(D + D') \\ &= A'B'C'D + A'B'C'D' + AB'CD' \\ &\quad + A'B'CD' + A'BCD' + AB'C'D \\ &\quad + AB'C'D' \\ &= \sum(0, 1, 2, 6, 8, 9, 10) \\ &= B'C' + B'D' + A'CD' \end{aligned}$$

AB \ CD	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

The blue group covers 4 corner
* corners are adjacent
⇒ always creat corner groups FIRST

Four-variable K-map



- Simplify the expression
 $F(A, B, C, D) = \sum(3, 4, 5, 7, 9, 13, 14, 15)$.
 - It may be noted that one quad can also be formed, but it is redundant as the squares contained by the quad are already covered by the pairs which are essential.
- $F = A'BC' + A'CD + AY'D + ABC$.

AB \ CD	00	01	11	10
00			1	
01	1	1	1	
11		1	1	1
10		1		

Four-variable K-map



- Simplify the expression $F(A, B, C, D) = \prod(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$.
 - The above expression is given in respect to the maxterms.
 - 0's are to be placed instead of 1's at the corresponding maxterm squares.
- $F = C(B' + D)$.


In maxterm.
 If $B=1$
 \Rightarrow write B'

connect B & D
 use "+"

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	0	1	0
11	0	0	1	0
10	0	0	1	1

while 1s represent minterms,
 0s represent maxterms.
 So we can group 0s instead
 of group 1s.

Simplification of POS

$$\textcircled{1} F(A, B, C, D) = \Pi (1, 2, 5, 7 \dots)$$


write a "0" in Kmap

$\textcircled{2}$ for the literals unchanged in a group.

$$\begin{cases} 0 \rightarrow A \\ 1 \rightarrow A' \end{cases}$$

$\textcircled{3}$ different literals in one group are connected by addition

$\textcircled{4}$ different groups are connected by multiplication

Four-variable K-map



- Simplify the expression $F(A, B, C, D) = \prod(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$.
 - The other way to achieve the minimized expression is to consider the 1's of the Karnaugh map.
- $F = CD + B'C = C(B' + D)$.

↓
group 0 and group 1
give the same result


AB \ CD	00	01	11	10
00	0	0	1	1
01	0	0	1	0
11	0	0	1	0
10	0	0	1	1

Five-variable K-map




will NOT be tested

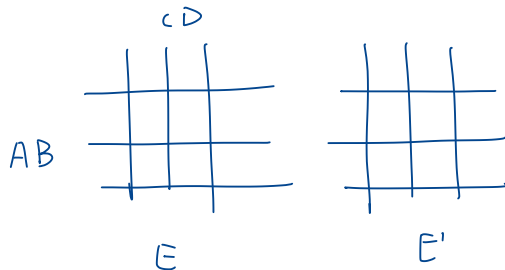- Karnaugh maps with more than four variables are not simple to use.
 - The number of cells or squares becomes excessively large and combining the adjacent squares becomes complex.
 - A five-variable Karnaugh map contains 2^5 or 32 cells.



Prime Implicants

- A *prime implicant* is a product term obtained by combining the maximum possible number of adjacent squares in the map.
- The prime implicants of a function can be obtained from the map by combining all possible maximum numbers of squares.
 - If a minterm in a square is covered by only one prime implicant, that prime implicant is said to be *essential*.
can NOT be remove
- Gate-level minimization:
 - Determine all essential prime implicants.
 - Find other prime implicants that cover remaining minterms.
 - Logical sum all prime implicants.

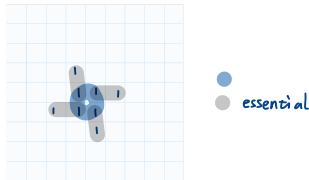



Don't care conditions

- In practice, Boolean function is **not specified** for certain combinations of input variables.
 - Input combinations never occur during the process of a normal operation.
 - Those input conditions are guaranteed never to occur.
- Such input combinations are called *don't-care conditions*.
- These input combinations can be plotted on the Karnaugh map for further simplification.
 - The don't care conditions are represented by d or X in a K-map.
 - They can be **either 1 or 0** upon needed.

and they are independent



Don't care conditions

- Simplify the expression $F(A, B, C, D) = \sum(1, 3, 7, 11, 15), d = \sum(0, 2, 5).$
→ function
- $F = A'B' + CD.$
→ don't care

AB \ CD	00	01	11	10
00	X	1	1	X
01		X	1	
11			1	
10			1	

→ 0/1



Don't care conditions

- Simplify the expression $F(A, B, C, D) = \sum(1, 3, 7, 11, 15), d = \sum(0, 2, 5)$.
- $F = A'D + CD$.

$$F(A, B, C, D) = \sum(0, 1, 2, 3) + d(4, 5)$$

$$F(A, B, C, D) = \prod(0, 1, 2) + d(4, 5)$$


are both okay.

AB \ CD	00	01	11	10
00	X	1	1	X
01		X	1	
11			1	
10			1	

More examples

- Using the Karnaugh map method obtain the minimal sum of the products expression for the function $F(A, B, C, D) = \sum(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$.

four variable

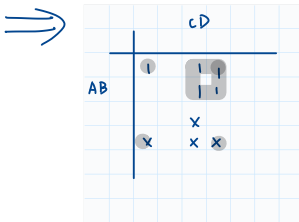

⇒ $B'D' + A'C$